

### Section 3.3 Assigned problems: 1-10.

1.  $10(1 - e^{-t/2})$
2.  $\frac{25}{2}e^{-t/10}(1 - e^{-2t/5})$
3.  $\frac{10}{17}(4e^{-t/2} - 4\cos(2t) + \sin(2t))$
4.  $\frac{10}{37}(-e^{-t/2} + \cos(3t) + 6\sin(3t))$
5.  $\frac{51}{5}(1 - e^{-t/2}) - \frac{t}{10}$
6.  $\frac{5}{2}(4 + e^{-t/2} - 5e^{-t/10})$
7.  $10(1 - e^{-t/10})$
8.  $te^{-t/10}$
9.  $\frac{50}{1 + 400\pi^2}(20\pi e^{-t/10} - 20\pi \cos(2\pi t) + \sin(2\pi t))$
10.  $\frac{40}{901}(-e^{-t/10} + \cos(3t) + 30\sin(3t))$
11.  $300(1 - e^{-t/10}) - 20t$
12.  $100(1 - e^{-t/20})^2$
13.  $CE(1 - e^{-t/(CR)})$
14.  $\frac{E}{R} + e^{-Rt/L}\left(I_0 - \frac{E}{R}\right)$
16. The current in the circuit is  $10e^{-t/20}(1 - e^{-t/20})$ . The maximum is  $5/2$  and occurs at time  $20 \ln 2 \approx 13.863$  seconds.
18. The general solution of the differential equation modeling this circuit is

$$c_1e^{-t/2} - \frac{2}{1 + 16\pi^2}(4\pi \cos(2\pi t) - \sin(2\pi t)).$$

Here  $c_1$  is an arbitrary constant. Since the function with  $c_1$  becomes negligible for large  $t$  the steady state response, that is the significant part of all solutions for large  $t$ , is

$$-\frac{2}{1+16\pi^2}(4\pi \cos(2\pi t) - \sin(2\pi t)).$$

The period of this function is 1. Hence its frequency is also 1.

20. By the capacitance law the voltage drop  $V(t)$  across a capacitor is related to the charge  $Q(t)$  on the capacitor by the following formula:  $Q(t) = CV(t)$ , where  $C$  is the capacitance, which is constant. Therefore  $Q'(t) = CV'(t)$ . Now we substitute the last two equations in

$$RQ'(t) + \frac{1}{C}Q(t) = E \cos(\omega t)$$

and get

$$RCV'(t) + \frac{1}{C}CV(t) = E \cos(\omega t)$$

which simplifies to

$$RCV'(t) + V(t) = E \cos(\omega t).$$

The general solution of the last differential equation is

$$V(t) = c_1 e^{-t/(RC)} + \frac{E}{1+(RC\omega)^2}(RC\omega \sin(\omega t) + \cos(\omega t)).$$

Here  $c_1$  is an arbitrary constant. As before, the function with  $c_1$  becomes negligible for large  $t$ . Therefore the steady state response, that is the significant part of all solutions for large  $t$ , is

$$\frac{E}{1+(RC\omega)^2}(RC\omega \sin(\omega t) + \cos(\omega t)).$$